


## Alternating Current

### Numerical Problems:

1. An iron cored coil of inductance  $3\text{H}$  and  $50\ \Omega$  resistance is placed in series with a resistor of  $550\ \text{ohm}$ , and a  $100\text{V}$ ,  $50\text{Hz}$  ac supply is connected across the arrangements. Find the current following in the coil and the voltage across the coil. [ $0.09\text{A}$ ,  $84.8\text{V}$ ]
2. An iron cored coil of inductance  $2\text{H}$  and  $50\ \Omega$  resistance is placed in series with a resistor of  $450\ \text{ohm}$ ,  $200\text{v}$ ,  $50\text{Hz}$  ac supply is connected across the arrangements. Find
  - i) the current following in the coil [ $0.25\text{A}$ ]
  - ii) the voltage across the coil. [ $15.75\text{V}$ ]
  - iii) The phase angle relative to the voltage supply. [ $51.3^\circ$ ]
3. A constant A.C. supply is connected to a series circuit consisting of a resistance of  $300\ \Omega$  in series with a capacitance  $6.67\ \mu\text{F}$ , the frequency of the supply being  $3000/2\ \pi\text{Hz}$ . It is desired to reduce the current in the circuit to half its value. Show how this could be done by placing an additional resistance. [Resistance to be added =  $306.1\ \text{ohm}$ ]
4. A circuit consists of capacitor of  $10\ \mu\text{F}$  and resistor of  $1000\ \Omega$ . An alternating emf of  $12\text{V}(\text{rms})$  and frequency  $50\text{Hz}$  is applied. Calculate the current flowing and voltage across the capacitor. [ $0.0114\text{A}$ ,  $3.63\text{V}$ ]
5. A circuit consists of a capacitor of  $2\ \mu\text{F}$  and a resistor of  $1000\ \Omega$ . An alternating emf of  $12\text{V}$  and frequency  $50\text{Hz}$  is applied. Find the voltage across the capacitor and the phase angle between the applied emf and the current. [ $10.2\text{V}$ ,  $57.9^\circ$ ]
6. An ac source of  $220\text{V}$ ,  $50\text{Hz}$  is connected to series circuit containing a resistor  $R$  and inductor  $L$  and a capacitor  $C$ . If  $R=200\ \Omega$ ,  $L=0.5\text{H}$  and  $C=10\ \mu\text{F}$ , calculate, (i) the current in the circuit, [ $0.856\text{A}$ ] (ii) the phase angle [ $-38.9^\circ$ ] and (iii) the power consumed in the circuit. [ $146.56\text{W}$ ]
7. A coil of inductance  $0.1\ \text{H}$  and negligible resistance is in series with a resistance  $40\ \Omega$ . A supply voltage of  $50\text{V}$  (rms) is connected to them, if the voltage across  $L$  is that across  $R$ , calculate the voltage across the inductor and frequency of the supply. [ $35.35\text{V}$ ,  $63.7\text{Hz}$ ]
8. L-C-R alternating current series circuit of  $L=1\text{H}$ ,  $C=1\ \mu\text{F}$ , and  $R=100\ \Omega$  are connected in series with a source of frequency  $50\text{Hz}$ . What is the phase shift between current and voltage? [ $88^\circ$ , voltage lags behind current]
9. A coil having inductance and resistance is connected to an oscillator giving a fixed sinusoidal output voltage of  $5\text{V}$  rms. With the oscillator set at a frequency of  $50\text{Hz}$ , the rms current in the coil is  $1\text{A}$  and at a frequency of  $100\text{Hz}$ , the rms current is  $0.625\text{A}$ . Determine the inductance of the coil. [ $0.0114\text{H}$ ]
10. A  $50\text{V}$  a.c. supply is connected to a resistor having resistance  $50\ \Omega$ , in series with a solenoid whose inductance is  $0.25\text{H}$ . The potential difference between the ends of the resistor is  $25\text{V}$ . Find the resistance of the wire of the solenoid. Take frequency of the ac source is  $50\text{Hz}$ . [ $11.89\ \text{ohm}$ ]
11. A  $50\text{V}$ ,  $50\text{Hz}$ , a.c. supply is connected to a resistor, of resistance  $40\ \Omega$ , in series with a solenoid whose inductance is  $0.20\text{H}$ . The p.d. between the ends of the resistor is found to be  $20\text{V}$ . What is the resistance of the wire of the solenoid? (Assume  $\pi^2=10$ ) [ $37.79\ \text{ohm}$ ]

12. A coil of inductance  $0.1\text{H}$  and negligible resistance is in series with a resistance  $R$ . A supply voltage of  $40\text{V(rms)}$  is connected to them. If a voltage across  $L$  is equal to that across  $R$ , calculate the voltage across  $R$  and the frequency of the supply? [ $28.3\text{V}$ ,  $63.7\text{Hz}$ ]
13. In a series LCR circuit,  $R=25\Omega$ ,  $L=30\text{mH}$  and  $C=10\mu\text{F}$  and these elements are connected to  $240\text{ ac (rms) } 50\text{Hz}$  source. Calculate the current in the circuit and voltmeter reading across a capacitor. [ $0.774\text{A}$ ,  $246.37\text{V}$ ]
14. An inductor, a resistor and capacitor are connected in series across an a.c. circuit. A voltmeter reads  $60\text{V}$  when connected across the inductor,  $16\text{V}$  across the resistor and  $30\text{V}$  across the capacitor:
  - i. What will the voltmeter read when placed across the series circuit? [ $34\text{V}$ ]
  - ii. What is the power factor of the circuit? [ $0.47$ ]
15. The maximum capacitance of a variable capacitor is  $33\text{pF}$ . What should be the self-inductance to be connected to this capacitor for the natural frequency of the LC circuit to be  $810\text{ KHz}$ . Corresponding to A.m. broadcast band of Radio Nepal? [ $1.17 \times 10^{-3}\text{H}$ ]
16. An alternating voltage  $10\text{V (rms)}$  and  $4\text{ kHz}$  frequency is applied to a resistor of resistance  $5\Omega$  in the series with a capacitor of capacitance  $10\mu\text{F}$ . Calculate the r.m.s. potential differences across the resistor and the capacitor. [ $7.8\text{V}$ ,  $6.2\text{V}$ ]
17. Alternative voltage in an ac circuit is represented by  $V=100\sqrt{2} \sin (100 \pi)$  volts. Find its roots mean square value and the frequency. [ $50\text{Hz}$ ]
18. A circuit consists an inductor of  $200\mu\text{ H}$  and the resistance of  $10\Omega$  in series with a variable capacitor and a  $0.10\text{V (r.m.s.)}$ ,  $1.0\text{ MHz}$  supply.
  - i. The capacitance to give resonance [ $1.26 \times 10^{-10}\text{F}$ ]
  - ii. The quality factor of the circuit at resonance [ $126$ ]
19. A  $100\text{V}$ ,  $50\text{Hz}$  AC source is connected to an LCR circuit containing  $L= 8.1\text{ mH}$ ,  $C=12.5\ \mu\text{ F}$  and  $R=10\Omega$  all connected in series. Find the potential difference across the resistor. [ $3.9\text{V}$ ]
20. A coil of inductance  $0.1\text{H}$  and negligible resistance is in series with a resistance  $40\Omega$ . A supply voltage of  $50\text{v (rms)}$  is connected to them. If the voltage across  $L$  is equal to that across  $R$ , calculate the voltage across the inductor and frequency of the supply. [ $R=35.35\text{volt}$ ,  $\text{Frequency}= 63.7\text{Hz}$ ]
21. A.C. mains of  $200\text{ volts}$  and  $50\text{Hz}$  is joined to a circuit containing an inductance of  $100\text{mH}$  and a resistance of  $20\Omega$  in series. Calculate the power consumed. [ $576.8\text{ Watt}$ ]
22. An iron cored coil of inductance  $2\text{H}$  and resistance  $50\Omega$  is connected in series with a resistor of  $950\Omega$ . A  $220\text{V}$ ,  $50\text{Hz}$  ac supply is connected across the arrangement. Find the current flowing in the circuit and the voltage across the coil. [ $\text{current}= 0.186\text{ampere}$  and  $\text{Voltage}=116.87\text{V}$ ]
23. A  $100\text{V}$ ,  $50\text{Hz}$  A.C. sources are connected to an LCR circuit Containing  $L=8.1\text{mH}$ ,  $C=12.5\ \mu\text{F}$  and  $R= 100\Omega$  all are connected in series. Find the p.d. across the resistor. [ $37\text{V}$ ]
24. An LCR series circuit, with  $L=0.12\text{H}$ ,  $C=7.3\ \mu\text{F}$  and  $R= 240\Omega$ , carries current of  $0.45\text{A}$  with a frequency of  $400\text{Hz}$ 
  - i. What are the phase angle and power factor? [ $\text{phase angle}= 45.57^\circ$  and  $\text{power factor}= 0.70$ ]

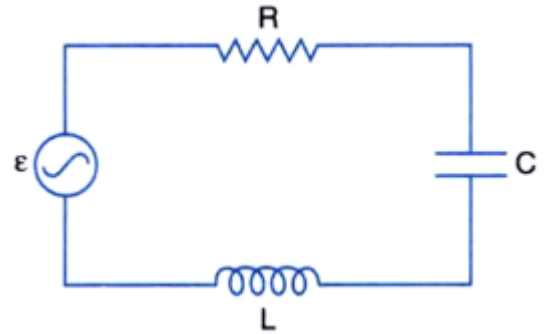- ii. What is impedance of the circuit? [344 $\Omega$ ]
25. A coil of inductance 0.5H and negligible resistance is in series with resistance of 40  $\Omega$ . A supply voltage of 40V (rms) is connected across them. If the voltage across the coil is equal to that across resistor, calculate the voltage across each component and frequency of the ac supply. [V across R= 35.35V, frequency= 12.74Hz]
26. Figure shows a series LCR circuit connected to a variable frequency 230 V source. L = 5.0 H, C = 80  $\mu$ F, R = 40 $\Omega$ .
- Determine the source frequency which drives the circuit in resonance. [1]
  - Obtain the impedance of the circuit and the amplitude of current at the resonating frequency. [2]
  - Determine the rms potential drops across the three elements of the circuit. [3]
  - Show that the potential drop across the LC combination is zero at the resonating frequency. [1]
  - How do you explain the observations that the algebraic sum of the voltages across the three elements is greater than the supplied voltages? [1]



## WORKED OUT EXAMPLE

**Example - 1.** An a.c. supply voltage is represented by the equation  $v = 220 \sqrt{2} \sin 100 \pi t$ . Determine (a) the peak voltage (b) the r.m.s. voltage (c) the angular frequency (d) the frequency (e) the period.

**Solution:**

The given equation  $V = 220 \sqrt{2} \sin 100 \pi t$  ..... (1)

The standard equation  $V = V_m \sin \omega t$  ..... (2)

Comparing equations (1) and (2) we get,

the peak voltage ( $V_m$ ) =  $220 \sqrt{2}$  V

$$V_{r.m.s.} = \frac{V_m}{\sqrt{2}} = \frac{220\sqrt{2}}{\sqrt{2}} = 220 \text{ V}$$

The angular frequency ( $\omega$ ) =  $100 \pi$

$$\text{Frequency (f)} = \frac{\omega}{2\pi} = \frac{100\pi}{2\pi} = 50 \text{ Hz}$$

$$\text{Time period (T)} = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ s}$$

**Example - 2.** An a.c. supply of frequency 50 Hz and voltage of 10 r.m.s is applied to (i) 5  $\Omega$  resistor (ii) 2H inductor and (iii) 1  $\mu\text{F}$  capacitor. Determine the r.m.s. current flowing in each case.

**Solution:**

i) R.m.s. voltage ( $V_{rms}$ ) = 10V

Resistance ( $R$ ) = 5  $\Omega$

$$\text{R.m.s. current (I}_{rms}) = \frac{V_{rms}}{R} = \frac{10}{5} = 2 \text{ A}$$

ii) Inductance ( $L$ ) = 2H,

**Solution:**

Here, Inductance ( $L$ ) = 0.1 H  
Resistance ( $R$ ) = 40  $\Omega$   
Voltage ( $V$ ) = 40 V

a) In LR circuit,

$$V_R^2 + V_L^2 = V^2$$

$$\therefore V_R = V_L$$

$$V_R^2 + V_R^2 = (40)^2$$

$$V_R^2 = \frac{(40)^2}{2} \text{ or } V_R = \frac{40}{\sqrt{2}}$$

or, Voltage across resistor ( $V_R$ ) =  $20 \sqrt{2} = 28.3$  V

$\therefore$  Voltage across inductor ( $V_L$ ) =  $V_R = 28.3$  V

b)  $\therefore V_L = V_R$

$$IX_L = IR \text{ where I is the current in the circuit}$$

$$\text{or, } X_L = R \text{ or } 2\pi fL = R$$

$$\text{Frequency (f)} = \frac{R}{2\pi L} = \frac{40}{2\pi \times 0.1} = 63.7 \text{ Hz.}$$

c) Power absorbed in the circuit = power absorbed in the resistor

$$= \frac{V_R^2}{R} = \frac{(20\sqrt{2})^2}{40} = \frac{20 \times 20 \times 2}{40} = 20 \text{ W}$$

**Example - 5.** A.C. mains of 220 volts, 50 cycles is joined to a circuit containing an inductance of 100 mH and a resistance of 20 ohms in series. Calculate the power consumed.

**Solution:**

Here, Voltage ( $V$ ) = 220 V  
Frequency ( $f$ ) = 50 cycles  
Inductance ( $L$ ) = 100mH = 0.1 H  
Resistance ( $R$ ) = 20  $\Omega$

$$\text{Impedance (Z)} = \sqrt{R^2 + (X_L)^2} = \sqrt{R^2 + (2\pi fL)^2}$$

$$= \sqrt{(20)^2 + (2\pi \times 50 \times 0.1)^2} = 37.24 \Omega$$

$$\text{Current (I)} = \frac{V}{Z} = \frac{220}{37.24} = 5.9 \text{ A}$$

$$\text{Power consumed } p = I^2 R = (5.9)^2 \times 20 = 698 \text{ W}$$

**Example - 6.** An iron cored coil of 2 H and 50  $\Omega$  resistance is placed in series with a resistor of 950  $\Omega$  and a 220V, 50 Hz a.c. supply is connected across the arrangement. Find (i) the current flowing in the circuit (ii) the voltage across the coil.

iii) Capacitance ( $C$ ) = 1  $\mu\text{F} = 10^{-6}$  F

$$I_{rms} = \frac{V_{rms}}{X_C} = \frac{V_{rms}}{\frac{1}{2\pi fC}} = V_{rms} \times 2\pi fC$$

$$= 10 \times 2\pi \times 50 \times 10^{-6} = 0.0031 \text{ A}$$

**Example - 3.** A circuit consisting of series arrangement of a resistor  $R$  of 20  $\Omega$ , an inductor  $L$  of 0.15 H and a capacitor  $C$  of 500  $\mu\text{F}$ . If an alternating current of 0.2 A (rms) and frequency  $\frac{100}{2\pi}$  Hz flows through the circuit, calculate the a.c. voltage (i) across each component, (ii) across  $R$  and  $L$  together (iii) across  $L$  and  $C$  together, (iv) the total voltage across L.C.R. What power is dissipated in each component?

**Solution:**

Here, Current ( $I$ ) = 0.2 A

$$\text{Frequency (f)} = \frac{100}{2\pi} \text{ Hz}$$

$$\text{Resistance (R)} = 20 \Omega$$

$$\text{Inductance (L)} = 0.15 \text{ H,}$$

$$\text{Capacitance (C)} = 500 \mu\text{F} = 500 \times 10^{-6} \text{ F}$$

i) Voltage across  $R$  ( $V_R$ ) =  $IR = 0.2 \times 20 = 4.0$  V

$$\text{Voltage across (V}_L) = IX_L = I \times 2\pi fL = 0.2 \times 2\pi \times \frac{100}{2\pi} \times 0.15 = 3 \text{ V}$$

$$\text{Voltage across C (V}_C) = IX_C = I \frac{1}{2\pi fC} = 0.2 \times \frac{1}{2\pi \times \frac{100}{2\pi} \times 500 \times 10^{-6}}$$

$$= 0.2 \times \frac{1}{0.05} = 4 \text{ V}$$

ii) Across  $R$  and  $L$  together

$$V^2 = V_L^2 + V_R^2$$

$$\text{or, } V = \sqrt{V_L^2 + V_R^2} = \sqrt{3^2 + 4^2} = 5 \text{ V}$$

iii) Across  $L$  and  $C$ ,  $V = V_C - V_L = 4 - 3 = 1$  V

iv) Across  $L$ ,  $C$ ,  $R$ :  $V = \sqrt{V_R^2 + (V_C - V_L)^2} = \sqrt{4^2 + 1^2} = 4.1$  V

$\therefore$   $L$  and  $C$  consumes no power. The power is dissipated only in the resistor.

$$\text{So, power dissipated in the resistor}$$

$$P = I^2 R = (0.2)^2 \times 20 = 0.8 \text{ W}$$

**Example - 4.** A coil inductance  $L$  and negligible resistance is in series with a resistance  $R$ . A supply voltage of 40 V (r.m.s.) is connected to them. If the voltage across  $L$  is equal to that across  $R$ , calculate (a) the voltage across each component (b) the frequency  $f$  of the supply (c) the power absorbed in the circuit if  $L = 0.1$  H,  $R = 40 \Omega$ .

**Solution:**

Here, in LR circuit as shown in the figure,  
Total resistance ( $R$ ) =  $950 + 50 = 1000 \Omega$

$$\text{Impedance (Z)} = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{R^2 + (2\pi fL)^2}$$

$$= \sqrt{(1000)^2 + (2\pi \times 50 \times 2)^2} = 1181 \Omega$$

$$\text{Current (I)} = \frac{V}{Z} = \frac{220}{1181} = 0.186 \text{ A}$$

The voltage across the coil

$$= IX_L = I \sqrt{r^2 + X_L^2} = I \sqrt{r^2 + (2\pi fL)^2}$$

$$= 0.186 \sqrt{(50)^2 + (2\pi \times 50 \times 2)^2} = 117.24 \text{ V}$$

**Example - 7.** A 50 V, 50 Hz a.c. supply is connected to a resistor, of resistance 40  $\Omega$  in series with a solenoid whose inductance is 0.2 H. The p.d. between the ends of the resistor is found to be 20 V. What is the resistance of the wire of the solenoid? (Given  $\pi^2 = 10$ )

**Solution:**

Here, Voltage ( $V$ ) = 50V

$$\text{Frequency (f)} = 50 \text{ Hz,}$$

$$\text{Inductance (L)} = 0.2 \text{ H,}$$

$$\text{Resistance (R)} = 40 \Omega$$

$$\text{Voltage across (V}_R) = 20 \text{ V}$$

Let  $r$  be the resistance of the solenoid. The impedance of the circuit,  $Z$ ,

$$Z = \sqrt{(R+r)^2 + X_L^2} = \sqrt{(40+r)^2 + 4\pi^2 f^2 L^2}$$

$$= \sqrt{(40+r)^2 + 4 \times 10 \times 2500 \times 0.04} = \sqrt{(40+r)^2 + 4000}$$

$$\text{The current through the circuit} = \frac{V_R}{R} = \frac{20}{40} = 0.5 \text{ A}$$

$$\text{Impedance of the circuit} = \frac{V}{I} = \frac{50}{0.5} = 100 \Omega$$

$$\therefore \sqrt{(40+r)^2 + 4000} = 100$$




$$\text{or, } (40+r)^2 + 4000 = 100$$

$$\text{or, } (40+r)^2 = 10,000 - 4000$$

$$\text{or, } (40+r)^2 = 6000 \text{ or } 40+r = 77.5$$

$$\text{or, } r = 37.5 \Omega$$

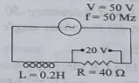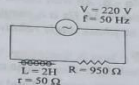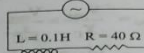Hence, the resistance of the wire of the solenoid is 37.5  $\Omega$ .



**Example - 8.** An iron cored coil of 2 H and 50 Ω resistance placed in series with a resistor of 450 Ω and a 100 V, 50 Hz a.c. supply is connected across the arrangement find (a) the current flowing in the coil, (b) its phase angle relative to the voltage supply, (c) the voltage across the coil.

**Solution:**

- (a) The reactance  $X_L = 2\pi fL = 2\pi \times 50 \times 2 = 628 \Omega$   
 Total resistance  $R = 50 + 450 = 500 \Omega$   
 Circuit impedance  $Z = \sqrt{X_L^2 + R^2} = \sqrt{628^2 + 500^2} = 803 \Omega$   
 $\therefore I = \frac{V}{Z} = \frac{100}{803} \text{ A} = 0.124 \text{ A}$
- (b)  $\tan \theta = \frac{X_L}{R} = \frac{628}{500} = 1.256$   
 So  $\theta = 51.5^\circ$
- (c) For the coil,  $X_L = 628 \Omega$  and  $R = 50 \Omega$   
 So coil impedance  $Z = \sqrt{X_L^2 + R^2} = \sqrt{628^2 + 50^2} = 630 \Omega$   
 Thus voltage across coil  $V = IZ = 0.124 \times 630 = 78.12 \text{ V}$ .

**Example - 9.** A circuit consists of capacitor of 2 μF and a resistor of 1000 Ω. An alternating e.m.f. of 12 V (r.m.s.) and frequency 50 Hz is applied. Find (1) the current flowing, (2) the voltage across the capacitor, (3) the phase angle between the applied e.m.f. and current, (4) the average power supplied.

**Solution:**

- In a CR circuit,  
 The reactance  $X_C$  of the capacitor is given by  
 $X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 2 \times 10^{-6}}$   
 $= 1592.35 \Omega$   
 $\therefore$  Total impedance  $Z = \sqrt{X_C^2 + R^2} = \sqrt{1000^2 + (1592.35)^2}$   
 $= 1880.31 \Omega$
- (1) Current,  $I = \frac{V}{Z} = \frac{12}{1880.31} = 6.4 \times 10^{-3} \text{ A}$
- (2) Voltage across C,  $V_C = IX_C = \frac{12}{1880.31} \times 1592.35 = 10.2 \text{ V}$
- (3) The phase angle  $\theta$  is given by  
 $\tan \theta = \frac{X_C}{R} = \frac{1592.35}{1000} = 1.59$

$$\begin{aligned} \therefore R_1 + r &= \sqrt{220 \times 110} \\ \text{or, } 100 + r &= 155.56 \\ \text{or, } r &= 55.56 \Omega \dots \dots \dots (2) \\ \text{Hence, } X_L &= 100 + 55.56 = 155.56 \\ \text{or, } 2\pi fL &= 155.56 \\ \therefore L &= \frac{155.56}{2\pi f} = \frac{155.56}{2\pi \times 60} = 0.413 \text{ H} = 413 \text{ mH.} \end{aligned}$$

**Example - 12.** A supply of 240 V and 50 Hz provides a current of 1.00 A to a coil of self inductance of 0.200 H and a resistance of 50 Ω and the current is in phase with the potential difference of the source. Find the values of the components that must be put in series with the coil.

**Solution:**

- Here, Inductance (L) = 0.200 H  
 Resistance (R) = 50.0 Ω  
 Current (I) = 1.0 A  
 Voltage (V) = 240 V  
 Frequency (f) = 50 Hz

In a LC circuit,

When the current is in phase with the potential difference, then

$$X = X_L - X_C = 0$$

$$Z = \sqrt{R^2 + X^2} = R$$

$$\text{But, } Z = \frac{V}{I} = \frac{240}{1} = 240 \Omega$$

$$\therefore R = 240 \Omega$$

$\therefore$  Resistance to be added in series =  $240 - 50 = 190 \Omega$

Again, for resonance,  $X_L = X_C$

$$\text{or, } 2\pi fL = \frac{1}{2\pi fC}$$

$$\text{or, } C = \frac{1}{4\pi^2 f^2 L} = \frac{1}{4\pi^2 (50)^2 \times 0.2} = 50.6 \times 10^{-6} \text{ F} = 50.6 \mu\text{F}$$

$\therefore$  The resistance of 190 Ω and a capacitor of 50.6 μF are connected in series with the coil to make in same phase.

**Example - 13.** A constant a.c. supply is connected to a series circuit consisting of a 300 Ω in series with a capacitance of 6.67 μF, the frequency of the supply being 3000/2π Hz. It is desired to reduce the current in the circuit to half its value. Show how this could be done by placing either (a) an additional resistance or (b) an inductance, in series. Calculate in each case the magnitude of the extra component.

(4) Average power supplied =  $I^2 R = \left(\frac{12}{1880.31}\right)^2 \times 1000 = 0.0407 \text{ W}$ .

**Example - 10.** A capacitor of capacitance C, a coil of inductance L and resistance R and a lamp are placed in series with an alternating voltage V. Its frequency f is varies from a low to a high value while the magnitude of V is kept constant. Describe and explain how the brightness of the lamp varies.


If  $V = 0.01 \text{ V}$  (r.m.s.) and  $C = 0.4 \mu\text{F}$ ,  $L = 0.4 \text{ H}$ ,  $R = 10 \Omega$  calculate (i) the resonant frequency, (ii) the maximum current, (iii) the voltage across C at resonance, neglecting the lamp resistance.

**Solution:**

When f is varied, the impedance Z of the circuit decreases to a minimum value (resonance) and then increase in Z is a minimum when  $X_L = X_C$ , so that  $Z = R$  at resonance. Since the current flowing in the circuit increases to a maximum and then decreases, the brightness of the lamp increases to a maximum at resonance and then decreases.

- (i) Resonant frequency  $f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.4 \times 0.4 \times 10^{-6}}} = \frac{10^3}{2\pi \times 0.4} = 396.08 \text{ Hz}$
- (ii) Maximum current =  $\frac{V}{R} = \frac{0.01}{10} = 0.001 \text{ A}$  (r.m.s.)
- (iii) Voltage across C =  $IX_C = 0.001 \times \frac{1}{2\pi \times 398 \times 0.4 \times 10^{-6}} = 1 \text{ V}$

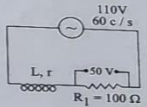**Example - 11.** A 110 V, 60 Hz a.c. generator was connected to a series combination 100 Ω resistor and an inductor as shown in figure. The voltage across the resistor is 50 V and voltage is found to be leading the current by 45°. What are the resistance and inductance of the inductor?



**Solution:**

$$\text{The current } I = \frac{\text{Voltage}}{R_1} = \frac{50}{100} = 0.5 \text{ A}$$

$$\text{Impedance of the circuit } Z = \frac{V}{I} = \frac{110}{0.5} = 220 \Omega$$

$$\text{But, } \tan \phi = \frac{V_L}{V_R} = \frac{X_L}{I(R_1 + r)} = \frac{X_L}{R_1 + r}$$


$$\text{or, } \tan 45^\circ = \frac{X_L}{R_1 + r}$$

$$\text{or, } X_L = R_1 + r \dots (i)$$

$$\text{Now, } Z = \sqrt{(R_1 + r)^2 + X_L^2}$$

$$\text{or, } 220 = \sqrt{(R_1 + r)^2 + (R_1 + r)^2}$$
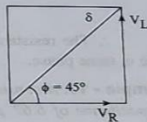
$$\therefore (R_1 + r)^2 = \frac{220 \times 220}{2} = 220 \times 110$$



Here, Resistance (R) = 300 Ω  
 Capacitance (C) = 6.67 μF  
 Frequency (f) =  $\frac{3000}{2\pi}$  Hz  
 Capacitive reactance ( $X_C$ ) =  $\frac{1}{2\pi fC} = \frac{1}{2\pi \times \frac{3000}{2\pi} \times 6.67 \times 10^{-6}}$   
 $= \frac{1000}{3 \times 6.67} = 50 \Omega$   
 Impedance (Z) =  $\sqrt{R^2 + X_C^2} = \sqrt{(300)^2 + (50)^2}$   
 $= 304.1 \Omega$   
 New impedance (Z') =  $2Z = 2 \times 304.1 = 608.2 \Omega$

a) Let  $R_1$  be the resistance to be added; then

$$Z' = \sqrt{(R + R_1)^2 + X_C^2}$$

$$\text{or, } (608.2)^2 = (300 + R_1)^2 + 2500$$

$$\text{or, } (300 + R_1)^2 = (608.2)^2 - 2500$$

$$= 369907.2 - 2500$$

$$= 367407.2$$

$$300 + R_1 = \sqrt{367407.2} = 606.1$$

$$\therefore R_1 = 606.1 - 300 = 306.1 \Omega$$

b) Let L be the inductance to be placed in series, then

$$Z' = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{or, } (608.2)^2 = (300)^2 + (X_L - 50)^2$$

$$\text{or, } (X_L - 50)^2 = (608.2)^2 - (300)^2$$

$$= 369907.2 - 90000$$

$$\text{or, } (X_L - 50)^2 = 279907.2$$

$$\text{or, } X_L - 50 = \sqrt{279907.2} = 529.06 \approx 529$$

$$\text{or, } X_L = 529 + 50 = 579$$

$$L = \frac{579}{2\pi f}$$

$$\text{or, } L = \frac{579}{2\pi \times \frac{3000}{2\pi}} = 0.193 \text{ H} = 193 \text{ mH}$$


**Example - 14.** A coil having inductance and resistance is connected to an oscillator giving a fixed sinusoidal output voltage of 5.00 V r.m.s. with the oscillator set at a frequency of 50 Hz the r.m.s. current

in the coil is 1.00 A and at a frequency of 100 Hz, the r.m.s. current is 0.625 A. (a) Determine the inductance of the coil (b) Calculate the ratio of the powers dissipated in the coil in the two cases.

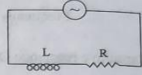**Solution:**

In LR circuit,

- Voltage (V) = 5.0V
- Frequency (f<sub>1</sub>) = 50 Hz
- Current (I<sub>1</sub>) = 1.0A
- Frequency (f<sub>2</sub>) = 100 Hz
- Current (I<sub>2</sub>) = 0.625 A



Impedance at frequency 50Hz is given by,

$$Z_1 = \frac{V}{I_1} = \frac{5}{1} = 5 \Omega$$

Impedance at frequency 100 Hz is given by,

$$Z_2 = \frac{V}{I_2} = \frac{5}{0.625} = 8 \Omega$$

Again,  $Z_1^2 = R^2 + \omega_1^2 L^2$   
 or,  $Z_1^2 = R^2 + 4\pi^2 f_1^2 L^2$   
 $Z_2^2 = R^2 + \omega_2^2 L^2$  ..... (i)

Similarly,  $Z_2^2 = R^2 + 4\pi^2 f_2^2 L^2$  ..... (ii)

Subtracting eq. (ii) from (i)

$$Z_2^2 - Z_1^2 = (4\pi^2 f_2^2 - 4\pi^2 f_1^2) L^2$$

or,  $L^2 = \frac{Z_2^2 - Z_1^2}{4\pi^2(f_2^2 - f_1^2)} = \frac{8^2 - 5^2}{4\pi^2[(100)^2 - (50)^2]}$   
 $= \frac{39}{4\pi^2 \times 7500} = \frac{39}{296088} = 0.000131717$

$\therefore L = 0.0114 \text{ H}$

- b) Power dissipated in the first case  $P_1 = I_1^2 R$   
 Power dissipated in the 2<sup>nd</sup> case  $P_2 = I_2^2 R$

$$\therefore \frac{P_1}{P_2} = \frac{I_1^2 R}{I_2^2 R} = \left(\frac{1.00}{0.625}\right)^2 = 2.56$$

**Example - 15.** An a.c. generator of constant 50 Vr.m.s. and a variable frequency is connected in series with a 2.0 Ω resistor, 5 H inductor and a 2.0 μF capacitor. The frequency is adjusted until the current in the circuit has a maximum value of 5 A r.m.s. Calculate the resistance of the wire of the inductor and the value of this frequency (Given π<sup>2</sup> = 10)

**Solution:**

For the maximum current,

Now, Power consumed (P) = IV cosθ = 120 × 0.8 ×  $\frac{R}{Z}$   
 $= 120 \times 0.8 \times \frac{75}{150} = 48 \text{ W}$

Hence, the power consumed in the circuit is 48 W.

**Example - 18.** A coil of inductance 0.1 H and negligible resistance is in series with a resistance 40 Ω. A supply voltage of 50 V (r.m.s) is connected to them. If the voltage across L is equal to that across R, calculate the voltage across the inductor and frequency of the supply.

**Solution:**

Here, inductance (L) = 0.1 H

Resistance (R) = 40 Ω

Supply voltage (V) = 50 V

Voltage across L = Voltage across R

1.  $X_L = R$

$L\omega = R$

or,  $2\pi fL = R$

$\therefore f = \frac{R}{2\pi L} = \frac{40}{2\pi \cdot 0.1} = 63.66 \text{ Hz}$

Again,  $Z = \sqrt{R^2 + X_L^2} = \sqrt{40^2 + (L2\pi f)^2} = 40\sqrt{2}$

Then  $I = \frac{V}{Z} = \frac{50}{40\sqrt{2}} = 0.884 \text{ A}$

Hence, the voltage across the inductor (L) = I. X<sub>L</sub>  
 $= 0.884 \times 2\pi \times 0.1 \times 63.66 = 35.4 \text{ V}$

**Example - 19.** A resistor of 100 Ω resistance and an inductor of 1 H inductance and a capacitor of 1 μF capacitance are placed in series with an a.c. source. Find the phase shift between current and voltage if the frequency of the a.c. supply is 50 Hz.

**Solution:**

Here,

Resistance of circuit (R) = 100Ω


Inductance of inductor (L) = 1 H

Capacitance of capacitor (C) = 1 μF = 10<sup>-6</sup> F

Frequency of the a.c. supply = 50 Hz

Now,

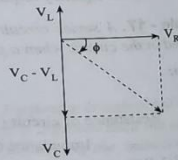Capacitive reactance (X<sub>C</sub>) =  $\frac{1}{2\pi fC}$   
 $= \frac{1}{2\pi \times 50 \times 10^{-6}} = 3183.09 \Omega$



$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{5 \times 2 \times 10^{-6}}}$$

$\therefore f = 50 \text{ Hz}$   
 Impedance of the circuit


$$Z = \frac{V}{I} = \frac{50}{5} = 10 \Omega$$

But,  $Z = \sqrt{(R+r)^2 + (X_L - X_C)^2}$

$$Z = \sqrt{(R+r)^2} = R+r$$

or,  $10 = 2 + r$

or,  $r = 8 \Omega$

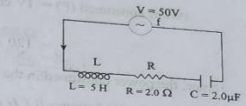

**Example - 16.** At what frequency would a 10 μF capacitor have reactance of 500 Ω?

**Solution:**

Here,

Capacitance of capacitor (c) = 10 μF = 10 × 10<sup>-6</sup> F

Reactance due to capacitor (X<sub>C</sub>) = 500 Ω

We know,  $X_C = \frac{1}{2\pi fC}$

or,  $500 = \frac{1}{2 \times \frac{22}{7} \times f \times 10 \times 10^{-6}}$

or,  $500 = \frac{7 \times 10^6}{2 \times 22 \times f \times 10}$

$\therefore f = \frac{7 \times 10^6}{500 \times 2 \times 22 \times 10} = 31.8 \text{ Hz}$

Hence,

The frequency required = 31.8 Hz

**Example - 17.** A series circuit has a resistance of 75 Ω and an impedance of 150 Ω. What power is consumed in the circuit when a p.d. of 120 V (r.m.s) is impressed across it?

**Solution:**

Here,

Resistance of circuit (R) = 75 Ω

Impedance (z) = 150 Ω

Potential difference applied (p.d) = 120V

Now, The current (I) =  $\frac{V}{Z} = \frac{120}{150} = 0.8 \text{ A}$

Inductive reactance (X<sub>L</sub>) = 2πfL = 2π × 50 × 1 = 314.15 Ω

Here, X<sub>C</sub> > X<sub>L</sub>

So, X<sub>C</sub> - X<sub>L</sub> = 3183.09 - 314.15 = 2868.98 Ω

Now, phase shift φ =  $\tan^{-1}\left(\frac{V_C - V_L}{V_R}\right) = \tan^{-1}\left(\frac{X_C - X_L}{R}\right)$   
 $= \tan^{-1}\left(\frac{2868.93}{100}\right) = 88^\circ$

So, current leads voltage by 88°.

**Example - 20.** Find the capacity of a capacitor which must be placed in series with a resistance of 50 ohm and inductance of 10 mH to bring the current in phase with the voltage, if the frequency of the a.c. supply be 50cycles/sec. What current will flow if 200 volts be impressed on the circuit?

**Solution:**

Here, Resistance (R) = 50 Ω

Inductance (L) = 10 mH = 10 × 10<sup>-3</sup> H

Frequency of a.c supply = 50 cycle/sec

Voltage applied (p. d) = 200 V

Now, Impedance (Z) =  $\sqrt{R^2 + X_L^2} = \sqrt{R^2 + (2\pi fL)^2}$   
 $= \sqrt{50^2 + \left(2 \times \frac{22}{7} \times 50 \times 10 \times 10^{-3}\right)^2} = 50.098 \Omega$

Now,  $I = \frac{V}{Z} = \frac{200}{50.098} = 4 \text{ A}$

Since, the frequency of a.c supply is same so,

$X_L = X_C$

or,  $2\pi fL = \frac{1}{2\pi fC}$

or,  $4 \times \frac{22^2}{7^2} \times 50^2 \times 10 \times 10^{-3} = \frac{1}{C}$

$\therefore C = 0.001 \text{ F}$

Capacitance of the capacitor is 0.001 F.

**Example - 21.** A series circuit consists of a resistor of 50 Ω an inductor of 10 mH and a capacitor of 10 μF. It is connected across a 200 V, 50 Hz line. What would a voltmeter read when it is connected across the resistor?

Here,

Resistance (R) = 50 Ω

So, Inductive reactance ( $X_L$ ) =  $2\pi f \times L = 2 \times \frac{22}{7} \times 50 \times 10 \times 10^{-3} = 3.1428 \Omega$

Capacitance ( $C$ ) =  $10 \mu\text{F} = 10 \times 10^{-6} \text{ F}$

So, capacitive reactance ( $X_C$ ) =  $\frac{1}{2\pi f C} = \frac{7 \times 10^6}{2 \times 22 \times 50 \times 10} = 318.18 \Omega$

Now, Impedance ( $Z$ ) =  $\sqrt{R^2 + (X_C - X_L)^2}$   
 $= \sqrt{50^2 + (318.18 - 3.1428)^2} = 318.98 \Omega$

So,  $I = \frac{V}{Z} = \frac{200}{318.98} = 0.626 \text{ A}$

Now, voltmeter reading across Resistance

$V = IR = 50 \times 0.626 = 31.3 \text{ V}$

**Example - 22.** A resistor  $5 \Omega$  is connected in series with an inductor of  $22 \text{ mH}$  and a capacitor of  $100 \mu\text{F}$  and a.c. supply of  $260 \text{ V}$ ,  $1000 \text{ Hz}$  (a) What is the power factor of the circuit (b) What is the power dissipated (c) What is the resonant frequency of the circuit.

**Solution:**

Here,

Voltage ( $V$ ) =  $260 \text{ V}$

Frequency ( $f$ ) =  $1000 \text{ Hz}$

Resistance of resistor ( $R$ ) =  $5 \Omega$

Inductance ( $L$ ) =  $22 \text{ mH} = 22 \times 10^{-3} \text{ H}$

Capacitance ( $C$ ) =  $100 \mu\text{F} = 100 \times 10^{-6} \text{ F}$

Now, Inductive reactance ( $X_L$ ) =  $2\pi f \times L = 2 \times \frac{22}{7} \times 1000 \times 22 \times 10^{-3}$   
 $= 138.2857 \Omega$

Capacitance reactance ( $X_C$ ) =  $\frac{1}{2\pi f C} = \frac{7 \times 10^6}{2 \times 22 \times 1000 \times 100}$   
 $= 1.5909 \Omega$

$\therefore$  Impedance ( $Z$ ) =  $\sqrt{R^2 + (X_L - X_C)^2} = \sqrt{9^2 + (138.285 - 1.5909)^2}$

Now, Current ( $I$ ) =  $\frac{V}{Z} = \frac{260}{137.05} = 1.9007 \text{ A}$

Power consumed in circuit =  $IV \cos\phi$

Now,  $\cos\phi = \frac{R}{Z}$

or,  $\cos\phi = \frac{5}{137.05} = 0.037$

Power dissipated =  $I V \cos\phi$

=  $1.9007 \times 260 \times 0.037$

=  $18.1 \text{ W}$

For LCR circuit

Resonant frequency ( $f$ ) =  $\frac{1}{2\pi\sqrt{LC}} = \frac{1}{2 \times \frac{22}{7} \times \sqrt{22 \times 10^{-3} \times 100 \times 10^{-6}}}$   
 $= 107.3 \text{ Hz}$

**Example - 23.** A  $110 \text{ V}$ ,  $100 \text{ W}$  lamp is to be run at  $220 \text{ V}$ ,  $53 \text{ cycle mains}$ . Calculate the inductance of the choke to be placed in series with the lamp?

**Solution:**

Here,

Voltage of the lamp ( $V$ ) =  $110 \text{ V}$

Power rated of the bulb ( $P$ ) =  $100 \text{ W}$

So,  $P = \frac{V^2}{R}$

or,  $R = \frac{V^2}{P} = \frac{110^2}{100} = 121 \Omega$

Also,  $V = IR$

or,  $110 = I \times R$

$\therefore$  Current in the circuit ( $I$ ) =  $0.90909 \text{ A}$

Since, the current to be used by the lamp remains the same, so,

$I = \frac{E_v}{Z}$

Where,  $E_v$  = Voltage across the combination of Resistance & Inductance  
 $Z$  = Impedance

$\therefore Z = 242 \Omega$

Also,  $Z = \sqrt{R^2 + X_L^2}$

or,  $(242)^2 = 121^2 + X_L^2$

or,  $X_L^2 = 242^2 - 121^2$

or,  $X_L^2 = 43923$

or,  $4 \times \left(\frac{22}{7}\right)^2 \times 53^2 \times L^2 = 43923$

$L^2 = \frac{43923}{4 \times \left(\frac{22}{7}\right)^2 \times 53^2}$

$\therefore L = 0.63 \text{ H}$

**Example - 24.** A coil having inductance  $10 \text{ mH}$  and resistance  $10 \Omega$  is connected across a  $220 \text{ V}$ ,  $50 \text{ Hz}$  line. Compute (i) the current in the coil (ii) the phase angle between the current and the supply voltage (iii) the power loss in the coil.

**Solution:**

Here,

Inductance of coil ( $L$ ) =  $10 \text{ mH} = 10 \times 10^{-3} \text{ H}$

Resistance ( $R$ ) =  $10 \Omega$

Inductive reactance ( $X_L$ ) =  $2\pi f L = 2 \times \frac{22}{7} \times 50 \times 10 \times 10^{-3}$   
 $= 3.143 \Omega$

$\therefore$  Impedance of circuit ( $Z$ ) =  $\sqrt{R^2 + X_L^2} = \sqrt{10^2 + (3.143)^2}$   
 $= 10.482 \Omega$

Hence, Current in the coil ( $I$ ) =  $\frac{V}{Z} = \frac{220}{10.482} = 20.99 \text{ A}$

For the phase angle between the current & voltage supply

$\tan\phi = \frac{X_L}{R} = \frac{3.143}{10}$

$\therefore \phi = 17.4^\circ$

Power loss in the coil =  $VI \cos\phi = 220 \times 21 \times \frac{R}{Z} = 220 \times 21 \times \frac{10}{10.482}$   
 $= 4407.55581 = 4407.56 \text{ W}$

**Example - 25.** An alternating voltage of r.m.s. value,  $283 \text{ V}$ ,  $50 \text{ Hz}$  is applied to a coil of  $20 \Omega$  resistance and  $10 \text{ mH}$  inductance. Find the r.m.s. current and angle by which the current lags behind the voltage.

**Solution:**

Here,

Voltage of a.c. supply ( $V$ ) =  $283 \text{ V}$

Frequency of a.c. supply ( $f$ ) =  $50 \text{ Hz}$

Resistance of coil ( $R$ ) =  $20 \Omega$

Inductance ( $L$ ) =  $10 \text{ mH} = 10 \times 10^{-3} \text{ H}$

$\therefore$  Inductive reactance ( $X_L$ ) =  $L\omega = 2\pi f L = 2 \times \frac{22}{7} \times 50 \times 10 \times 10^{-3}$   
 $= 3.143 \Omega$

Now, Impedance of circuit ( $Z$ ) =  $\sqrt{R^2 + X_L^2}$   
 $= \sqrt{20^2 + 3.143^2} = 20.245 \Omega$

So, R.M.S. current ( $I_{\text{rms}}$ ) =  $\frac{V_{\text{rms}}}{Z} = \frac{283}{20.245} = 13.97 \text{ A}$

Also,  $\tan\phi = \frac{X_L}{R}$

or,  $\tan\phi = \frac{3.143}{20}$

$\therefore \phi = 8.9^\circ$

Hence, the current lags behind the voltage by ( $8.9^\circ$ ).

**Example - 26.** A resistor of  $50 \Omega$ , an inductor of  $10 \text{ mH}$  and a capacitor of  $1 \mu\text{F}$  is connected to an a.c. source of variable frequency. At what frequency the current will be maximum in the circuit? What is the value of maximum current if the supply voltage is  $12 \text{ V}$ ?

**Solution:**

Resistance of resistor ( $R$ ) =  $50 \Omega$

Inductance of inductor ( $L$ ) =  $10 \text{ mH} = 10 \times 10^{-3} \text{ H}$

Capacitance of capacitor ( $C$ ) =  $1 \mu\text{F} = 1 \times 10^{-6} \text{ F}$

For the maximum value of frequency of a.c. supply we know

$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2 \times \frac{22}{7} \sqrt{10 \times 10^{-3} \times 1 \times 10^{-6}}} = 1591 \text{ Hz}$

Now, inductive reactance ( $X_L$ ) =  $2\pi f L = 2 \times \frac{22}{7} \times 1591 \times 10 \times 10^{-3} = 100 \Omega$

Capacitive reactance ( $X_C$ ) =  $\frac{1}{2\pi f C} = \frac{7 \times 10^6}{2 \times 22 \times 1591 \times 1} = 99.994 \Omega$

Hence, Impedance of circuit ( $Z$ ) =  $\sqrt{R^2 + (X_L - X_C)^2} = \sqrt{50^2 + (100 - 99.994)^2}$   
 $= 50.00006$   
 $Z \approx 50 \Omega$

Now, Value of maximum current supply ( $I$ ) =  $\frac{V}{Z} = \frac{12}{50} = 0.24 \text{ A}$

**Example - 27.** A resistor of  $48 \Omega$  and an inductor of  $\frac{7}{50\pi} \text{ H}$  are connected to an a.c. source of  $200 \text{ V}$ ,  $50 \text{ Hz}$ . Calculate (a) the peak voltage (b) the r.m.s. current (c) the r.m.s. voltage across the coil.

**Solution:**

Here,

Resistance of resistor ( $R$ ) =  $48 \Omega$

$$\text{Inductance of inductor (L)} = \frac{7}{50\pi} \text{ H}$$

$$\text{So, Inductive reactance (X}_L\text{)} = 2\pi fL = 2\pi \times 50 \times \frac{7}{50\pi} = 14\Omega$$

$$\text{Impedance of circuit (z)} = \sqrt{R^2 + X_L^2} = \sqrt{48^2 + 14^2} = 50\Omega$$

The peak voltage of a circuit is given by

$$V_o = \sqrt{2} V = \sqrt{2} \times 200 = 283 \text{ V}$$

Now, peak current of the circuit is given by

$$I_o = \frac{V_o}{z} = \frac{283}{50} = 5.66 \text{ A}$$

But, the r.m.s. current ( $I_r$ ) =  $0.707 \times I_o = 0.707 \times 5.66 = 4 \text{ A}$

The r.m.s voltage across the coil of inductive reactance ( $V_L$ ) =  $I_r X_L$   
=  $4 \times 14 = 56 \text{ V}$

**Example - 28.** An alternating e.m.f. of 6.0 V (r.m.s.) and frequency 50 Hz is applied to a circuit consisting a capacitor of 2  $\mu\text{F}$  and a resistor of 500.0  $\Omega$  in series (i) Find the current flowing (ii) the voltage across the capacitor (iii) the phase angle between the applied e.m.f. and current (iv) the average power supplied.

**Solution:**

Here,

R. M. S voltage of a.c supply ( $V_{rms}$ ) = 6.0 V

Frequency of an a.c supply ( $f$ ) = 50 Hz

Capacitance of capacitor ( $c$ ) =  $2\mu\text{F} = 2 \times 10^{-6} \text{ F}$

$$\therefore \text{Capacitance reactance (x}_c\text{)} = \frac{1}{2\pi fc} = \frac{1}{2 \times 22 \times 50 \times 2} = \frac{7 \times 10^6}{2 \times 22 \times 50 \times 2} = 1590.909 \Omega$$

Resistance ( $R$ ) = 500  $\Omega$

$$\therefore \text{Impedance (z)} = \sqrt{X_c^2 + R^2} = \sqrt{1590.909^2 + 500^2} = 1667.63 \Omega$$

$$\text{So, the current flowing the circuit (I)} = \frac{V}{z} = \frac{6}{1667.63} = 3.6 \times 10^{-3} \text{ A} = 3.6 \text{ mA}$$

Also, the voltage across the capacitor ( $V_c$ ) =  $I \times X_c = 3.6 \times 10^{-3} \times 1590.909 = 5.7 \text{ V}$

The phase angle between the applied e.m.f. and current

$$\tan\phi = \frac{X_c}{R} = \frac{1590.909}{500}$$

$$\therefore \tan\phi = 3.1818$$

$$\text{or, } P = I_{rms} \times z \times I_{rms} \times \frac{R}{z}$$

$$\text{or, } P = I_{rms}^2 \times R$$

$$\text{or, } 10.0 = 0.5^2 \times R$$

$$\therefore R = 40 \Omega$$

$$\text{Now, Impedance of the circuit (Z)} = \sqrt{R^2 + X_L^2} = \sqrt{40^2 + 25^2} = 47.16 \Omega$$

**Example - 31.** An inductor, a resistor and a capacitor are connected in series across an a.c. circuit A voltmeter reads 60 V when connected across the inductor, 16 V across the resistor and 30 V across the capacitor (i) What will the voltmeter reading when placed across the series circuit (ii) What is the power factor of the circuit?

**Solution:**

Here,

Inductor, capacitor and resistor are connected in series across an a.c. circuit

**Across the inductor**

Reading of Voltmeter ( $V_L$ ) = 60V

We know,  $V = IX_L$

or,  $60 = I \times X_L$  where  $X_L$  is the inductive reactance

$$\therefore X_L = \frac{60}{I}$$

**Across the resistor**

Reading of voltmeter ( $V_R$ ) = 16 V

We know,  $V = IR$

or,  $16 = IR$

$$\therefore R = \frac{16}{I}$$

**Across the capacitor**

Reading of voltmeter ( $V_C$ ) = 30V

We know,  $V = IR$  Where  $X_C$  is the capacitive reactance

or,  $30 = IX_C$

$$\therefore X_C = \frac{30}{I}$$

$$\begin{aligned} \text{Impedance of circuit (z)} &= \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{\left(\frac{16}{I}\right)^2 + \left(\frac{60}{I} - \frac{30}{I}\right)^2} \\ &= \sqrt{\frac{1}{I^2} \{6^2 + (60 - 30)^2\}} = \frac{1}{I} \sqrt{256 + 900} = \frac{34}{I} \end{aligned}$$

$$\therefore \phi = 72.6^\circ$$

$$\begin{aligned} \text{So, the average power supplied} &= IV \cos\phi \\ &= 3.6 \times 10^{-3} \times 6 \times \cos 72.6 \\ &= 6.47 \times 10^{-3} \text{ W} \\ &= 6.47 \text{ mW} \end{aligned}$$

**Example - 29.** A 100  $\Omega$  resistor, 1  $\mu\text{F}$  capacitor and a 0.1 H inductor are in series with an a.c. voltage of 6.0 V (r.m.s.). Its frequency is kept constant and it frequency is varied from a low to a high value resonance.

**Solution:**

Here, in LR circuit,

Inductance of inductor ( $L$ ) = 0.1 H

Capacitance of capacitor ( $C$ ) =  $1\mu\text{F} = 10^{-6} \text{ F}$

Resistance ( $R$ ) = 100  $\Omega$

(a) If  $f$  denotes the resonance frequency then

$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2 \times 22 \times \sqrt{0.1 \times 10^{-6}}} = 503 \text{ Hz}$$

$$\text{Now, inductive reactance (X}_L\text{)} = 2\pi fL = 2 \times \frac{22}{7} \times 503 \times 0.1 = 316.17\Omega$$

$$\text{Capacitive reactance (X}_C\text{)} = \frac{1}{2\pi fc} = \frac{1}{2 \times 22 \times 503} = 316.28 \Omega$$

$$\begin{aligned} \therefore \text{Impedance of the circuit (z)} &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{100^2 + (316.17 - 316.28)^2} = 100.36 \Omega \end{aligned}$$

$$(b) \therefore \text{The maximum current (I)} = \frac{V}{z} = \frac{6}{100.36} = 0.06 \text{ A}$$

$$(c) \text{The voltage across the capacitor (V}_1\text{)} = IX_C = 0.06 \times 316.28 = 18.9 \text{ V}$$

**Example - 30.** An inductance coil having a reactance of 25  $\Omega$  gives off heat at the rate of 10.0  $\text{J s}^{-1}$  when it carries a current of 0.5 A (r.m.s.), what is the impedance of the coil.

**Solution:**

Here,

Inductive reactance of the coil ( $X_L$ ) = 25  $\Omega$

Power consumed or heat produced per sec ( $P$ ) = 10.0 W

Current supplied ( $I_{rms}$ ) = 0.5 A

We know,

$$P = VI \cos\phi$$

$$P = V_{rms} I_{rms} \cos\phi$$

Now, the voltage across the a.c. circuit ( $V$ ) =  $IZ$

$$\text{or, } V = I \times \frac{34}{I}$$

$$\therefore V = 34 \text{ V}$$

$$\text{Power factor of the circuit (cos}\phi\text{)} = \frac{R}{z} = \frac{16}{34} = 0.47$$

**Example - 32.** A radio can tune over the frequency of a portion of MW broadcast band (880 KHz to 1500 KHz). If its L.C. circuit has an effective inductance of 400  $\mu\text{H}$ , what would be the range of its variable capacitor?

**Solution:**

Here,

Effective inductance ( $L$ ) = 200  $\mu\text{H} = 200 \times 10^{-6} \text{ H}$

Frequency of broadcast band ( $f$ ) = 880 KHz to 1500 KHz

**For, 880 KHZ**

$$\text{Effective frequency (f)} = \frac{1}{2\pi\sqrt{LC}}$$

$$880 \times 1000 = \frac{1}{2 \times 22 \sqrt{400 \times 10^{-6} \times C_1}}$$

$$C_1 = \frac{49 \times 10^6}{2^2 \times 22^2 \times 880^2 \times 1000^2 \times 400} = 8.17 \times 10^{-11} \text{ F}$$

**For 1200 KHZ**

$$\text{Effective frequency (f)} = \frac{1}{2\pi\sqrt{LC}}$$

$$1200 \times 1000 = \frac{1}{2 \times 22 \sqrt{400 \times 10^{-6} \times C_2}}$$

$$C_2 = \frac{49 \times 10^6}{4 \times 22^2 \times 1200^2 \times 1000^2 \times 400} = 4.394 \times 10^{-11} \text{ F}$$

Hence, the range of its variable capacitor will be

$$4.394 \times 10^{-11} \text{ F to } 8.17 \times 10^{-11} \text{ F.}$$